
Proabot Boat Circuit Design - Spring18 final

Circuit Design:

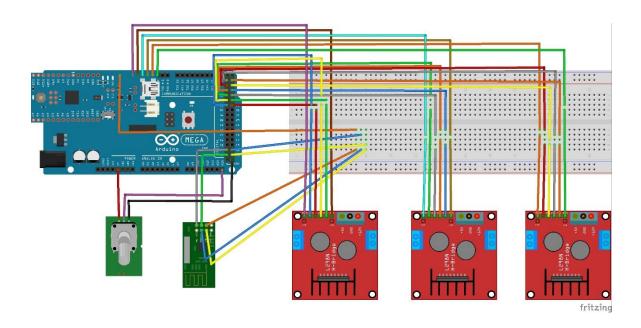


Components:


Arduino Mega 2560 L298N H-bridge DC motor driver *3 NRF24 Potentiometer


L298N H-bridge

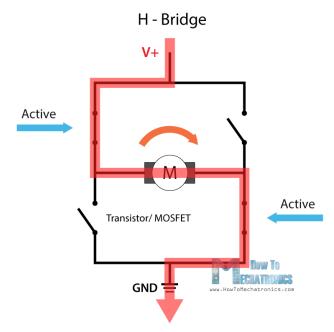Data Sheet: https://www.sparkfun.com/datasheets/Robotics/L298_H_Bridge.pdf H-bridge:



L298N pins:

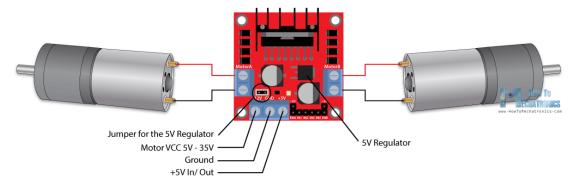

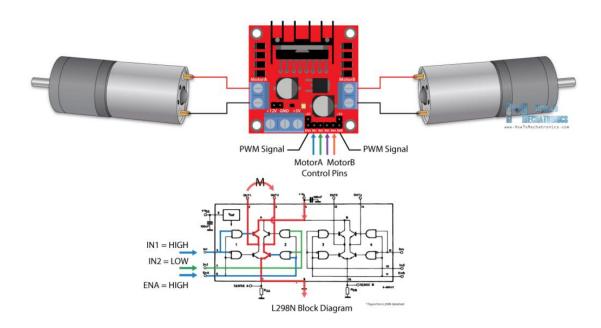

// The circuit uses 3 L298N to drive 6 motors.